

Battery Management System

Beia Cabrera Sanchez

What is a BMS

A Battery Management System (BMS) is a crucial component in managing the safety, health, and performance of batteries. It monitors key parameters like cell voltage, temperature, and charge levels to ensure the battery operates within safe limits. By preventing conditions such as overcharging, overheating, and voltage imbalances, the BMS helps protect the battery from damage and ensures optimal performance and longevity.

3 major components to BMS

1 | Temperature Sensing

Reads voltage changes across the thermistor to track temperature variations in each battery cell, ensuring they stay within safe operational limits to prevent thermal issues and extend battery life.


2 | Voltage Sensing

Detects and compare voltage levels across battery cells by taking the difference of $V+$ and $V-$. Continuously ensures that no cell within the battery pack exceeds its upper voltage limit or falls below its lower voltage limit, which is important for safety and battery health.

3 | Cell Balancing

Using MOSFETs transistor switches we can control voltage levels, when the BMS detects a particular cell has a higher voltage comparatively, it can activate its switch to allow some charge to drain, thus lowering voltage of that cell to match/equalize


General Overview of BMS

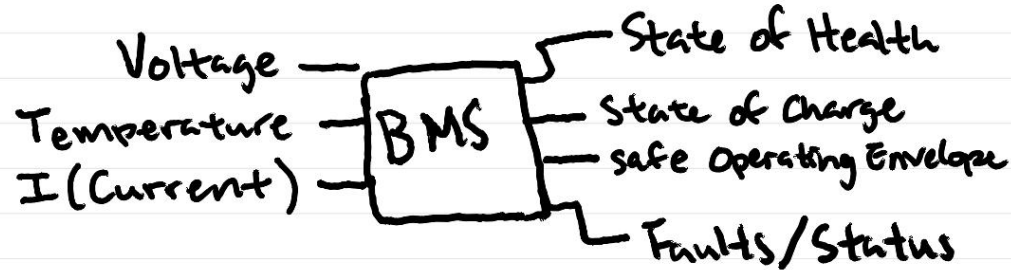

SOE: allows me to know how much
current charge/discharge
at any given time
w/ MOSFET transistor

Faults/Status signals from my Transceiver CANbus
allows MCU and other components to communicate
(CAN High, CAN Low)

BMS

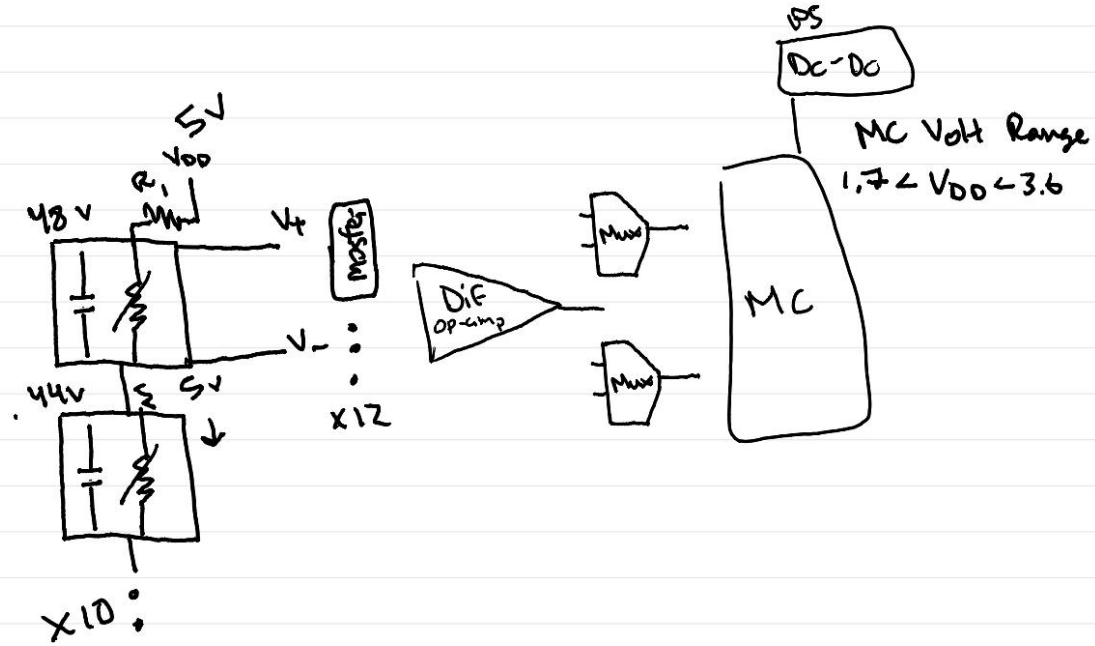

Battery Module


...as the first component :)

Li-ion building block Li4P2



Battery: Li₄P₂₅RT

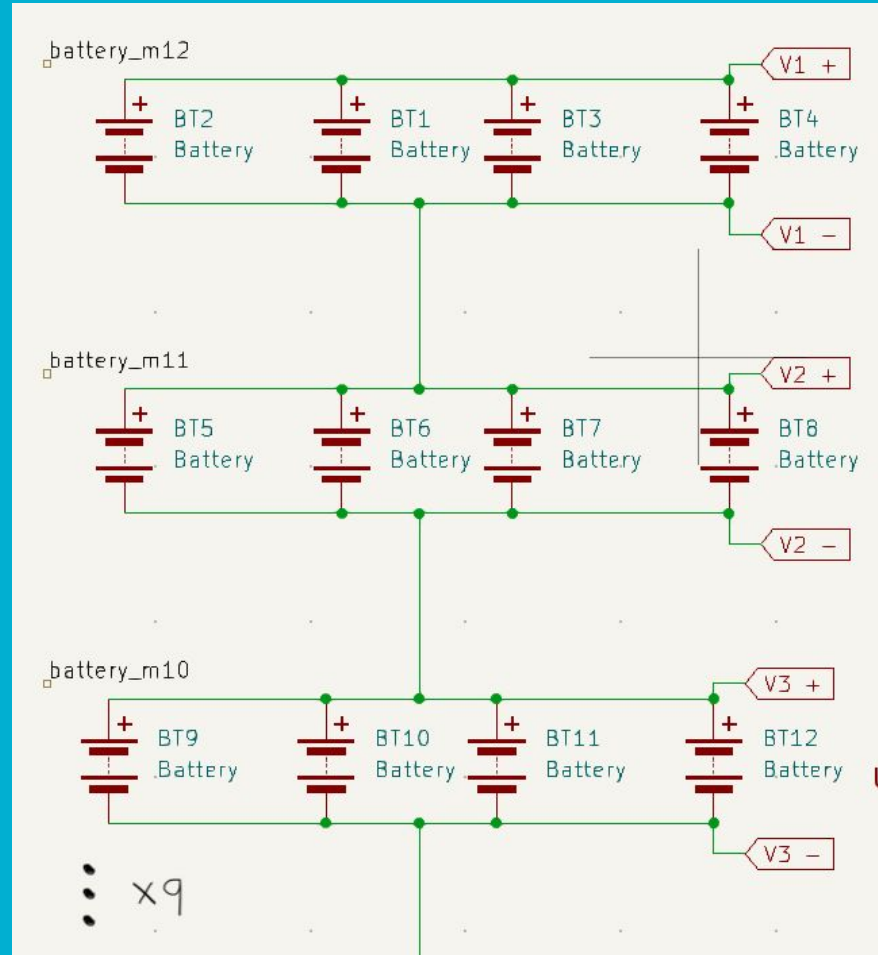- 12 series, 4 parallel battery module (12s4p)
- V_{max}: 4.2, V_{min}: 2.5 voltage per individual battery
- V_{max}: 50.4, V_{min}: 30V entire battery module
- Rechargeable




Temperature Sensing


Temperature sensing voltage divider is next to each battery cell in the casing to gauge a temperature

Voltage divider takes the voltage drop across the 5V ideal power supply to allow room for a lesser voltage V_{out} . Thermistor resistance changes according to temperature

$$V_{out} = \frac{R_t}{R + R_t} (V_s)$$

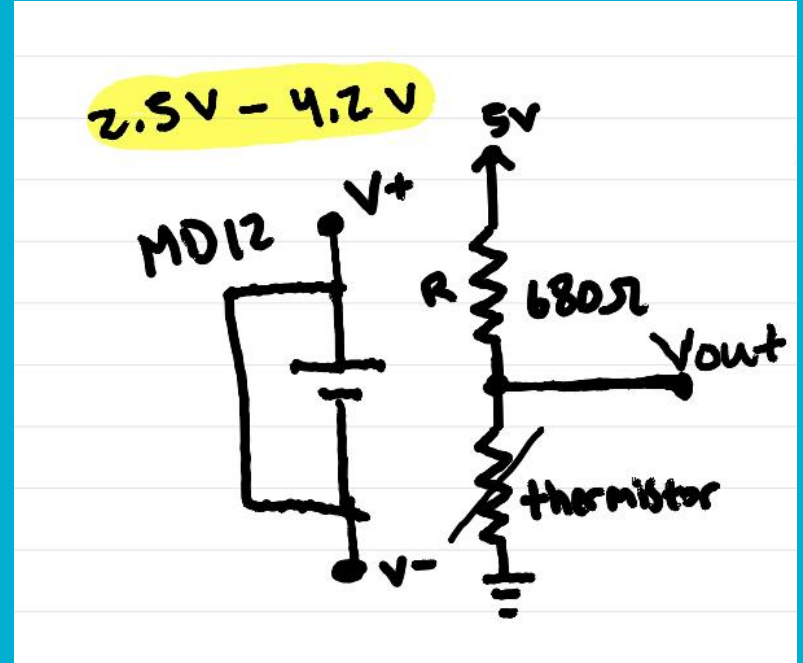

Temperature Sensing

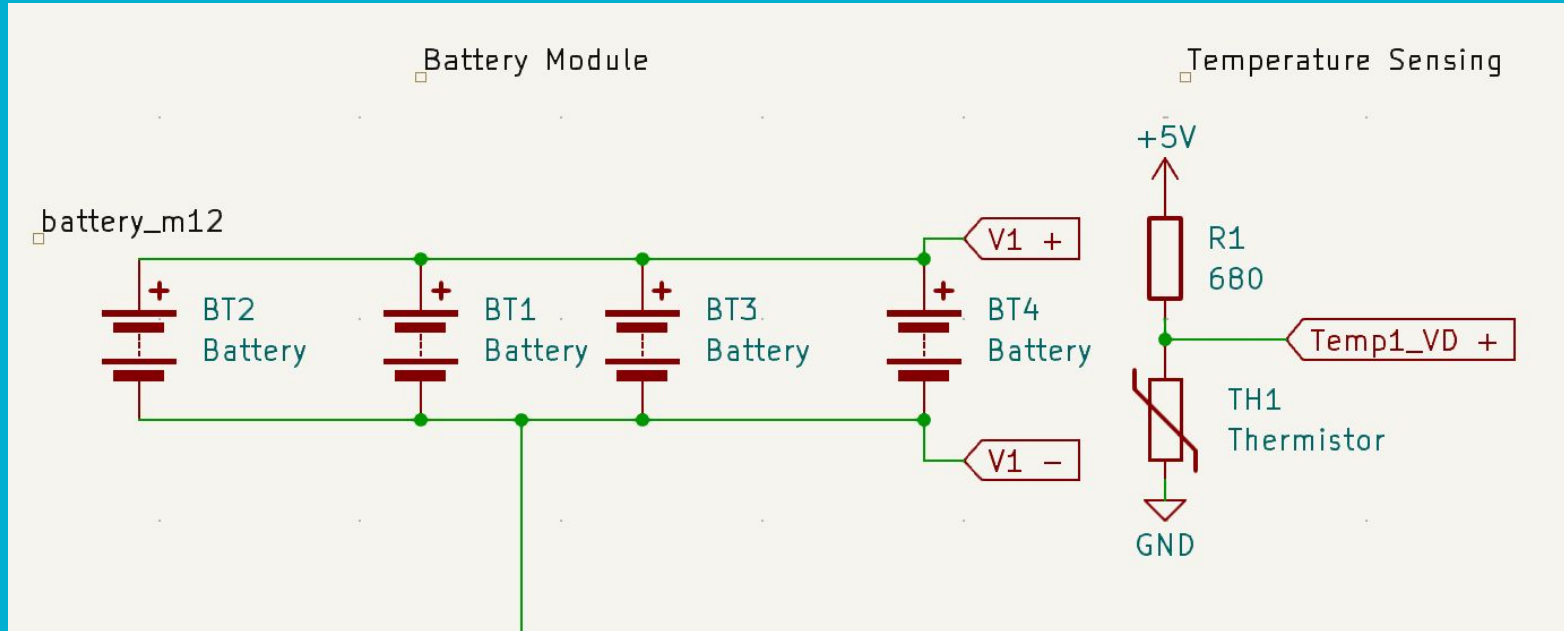

Cell Balancing w/ MOSFET Transistor

- 2N7002NXAK (NMOS)
- Operates based on the gate-source voltage V_{gs} . It turns on when V_{gs} exceeds a threshold range allowing current to flow between the drain and source allowing power distribution through its switch (connects or disconnects battery cells to balance charge or prevent excessive discharge)

FET Type	N-Channel
Technology	MOSFET (Metal Oxide)
Drain to Source Voltage (V_{dss})	60 V
Current - Continuous Drain (I_d) @ 25°C	190mA (T_a), 300mA (T_c)
Drive Voltage (Max Rds On, Min Rds On)	5V, 10V
Rds On (Max) @ I_d , V_{gs}	4.50hm @ 100mA, 10V
<u>$V_{gs(th)}$ (Max) @ I_d</u>	<u>2.1V @ 250μA</u>
<u>Gate Charge (Q_g) (Max) @ V_{gs}</u>	0.43 nC @ <u>4.5 V</u>
<u>V_{gs} (Max)</u>	<u>±20V</u>
Input Capacitance (C_{iss}) (Max) @ V_{ds}	20 pF @ 10 V

Passive Cell Balancing ->


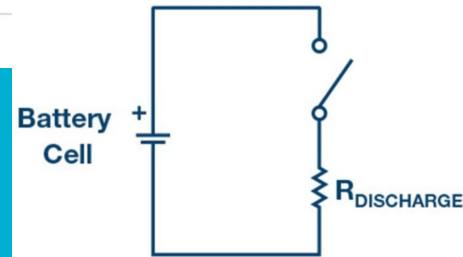


Figure 1. Passive cell balancer with bleed resistor.



Cell Balancing w/ MOSFET Transistor

Cell Balancing w/ Transistor Switch

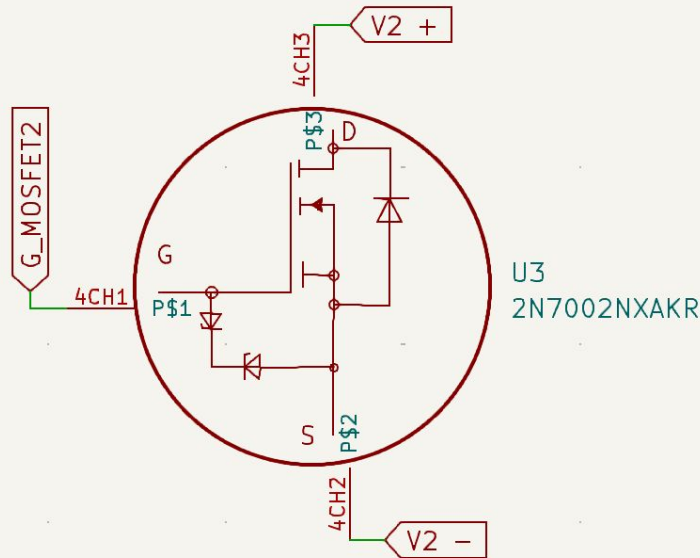

Transistor Switch Model: x12

NMOS:

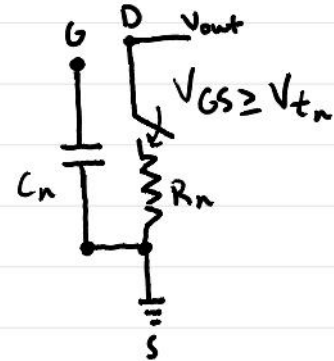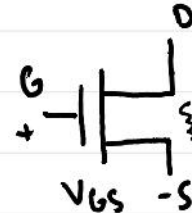

$$V_{GS(max)} = \pm 20$$


$$V_{tn} = 1V - 2.5V$$

$$V_G = 4.5 \quad V_{tn} = 2.1V$$


$4.5 \geq 2.1 \rightarrow$ MOSFET switch is on (closed)

Voltage Sensing

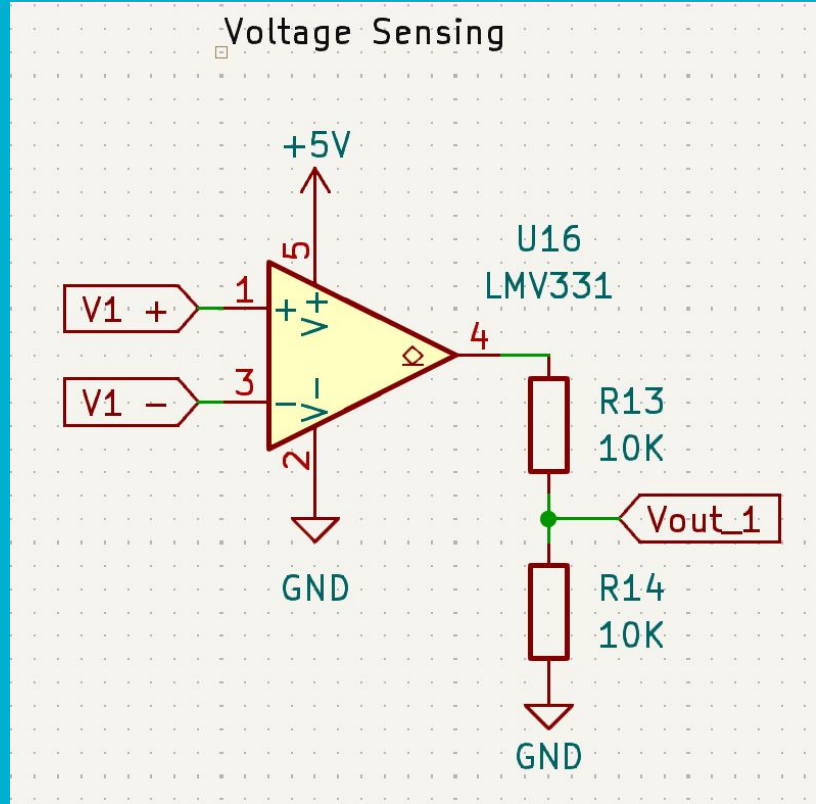
Differential Op-Amp outputs the voltage difference between two voltage inputs used for voltage reading. Using a voltage divider we can scale down the max supply voltages (5V) to output a voltage with room for the MCU voltage range of 1.7 - 3.6 V, we don't want a high voltage for MCU since we don't want to over supply it



Voltage Sensing

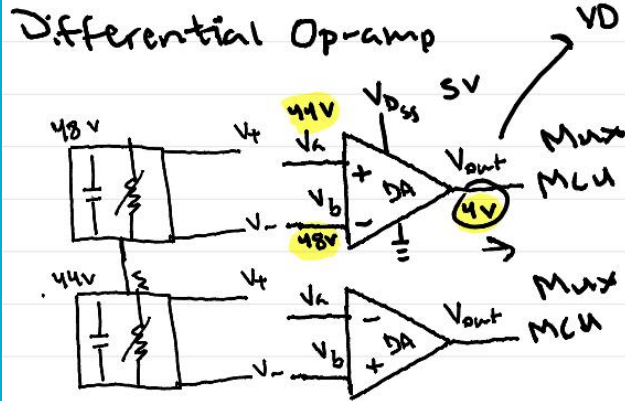


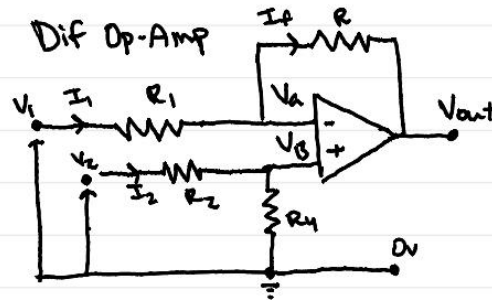
* we want to use high voltage of $\sim 56V$ (max)
 Since all the voltages from the battery pack in series stack so we are taking the difference
 $48V - 44V = 4V$
 $\therefore 44 - 40 = 4V$
 and so forth



Multiplexers


- Used to condense the number of outputs that came from all my temperature sensing reading (12 outputs from each of the components)
- Used to condense all the outputs from my voltage sensing Op-amps
- 16:1 ratio muxer w/ $2^4 \rightarrow 4$ selector bits which are 1, 0 binary values that essentially the MCU determine to output the proper reading from the inputs
- Supplied with a 3.3 V

Condensing the Number of Analog Inputs

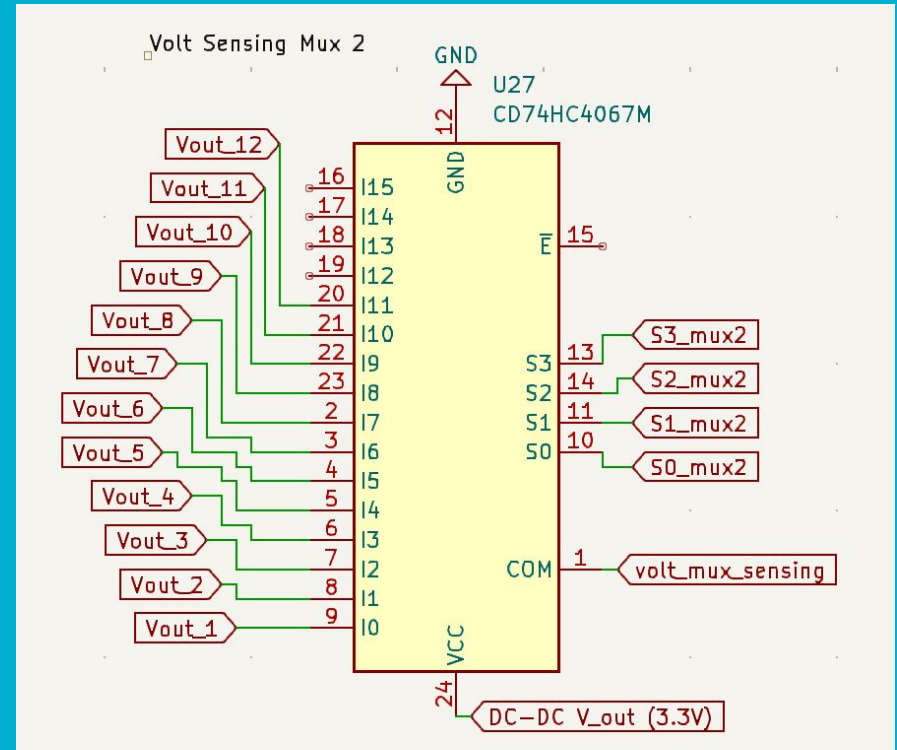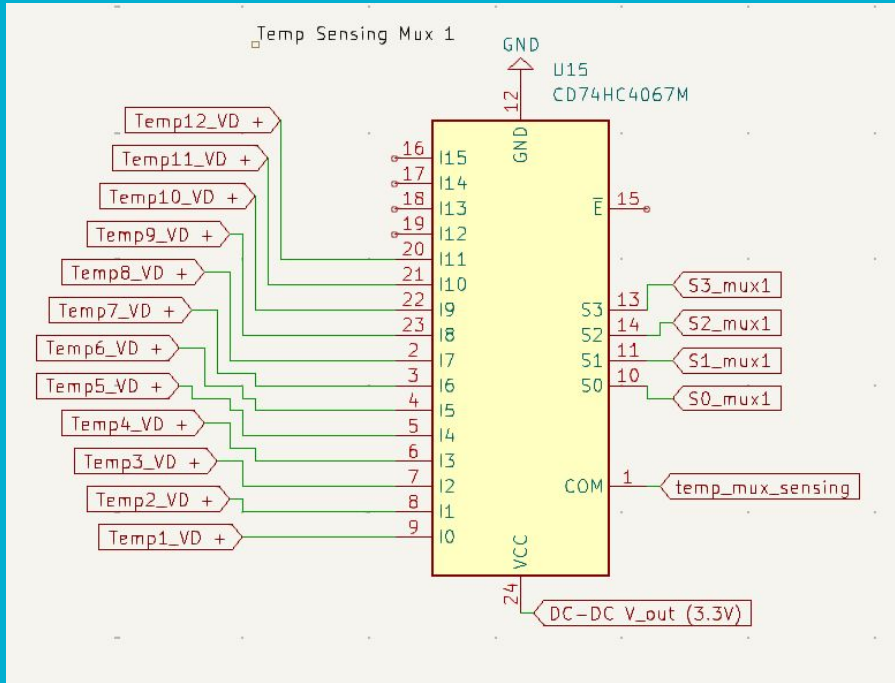

Microcontroller

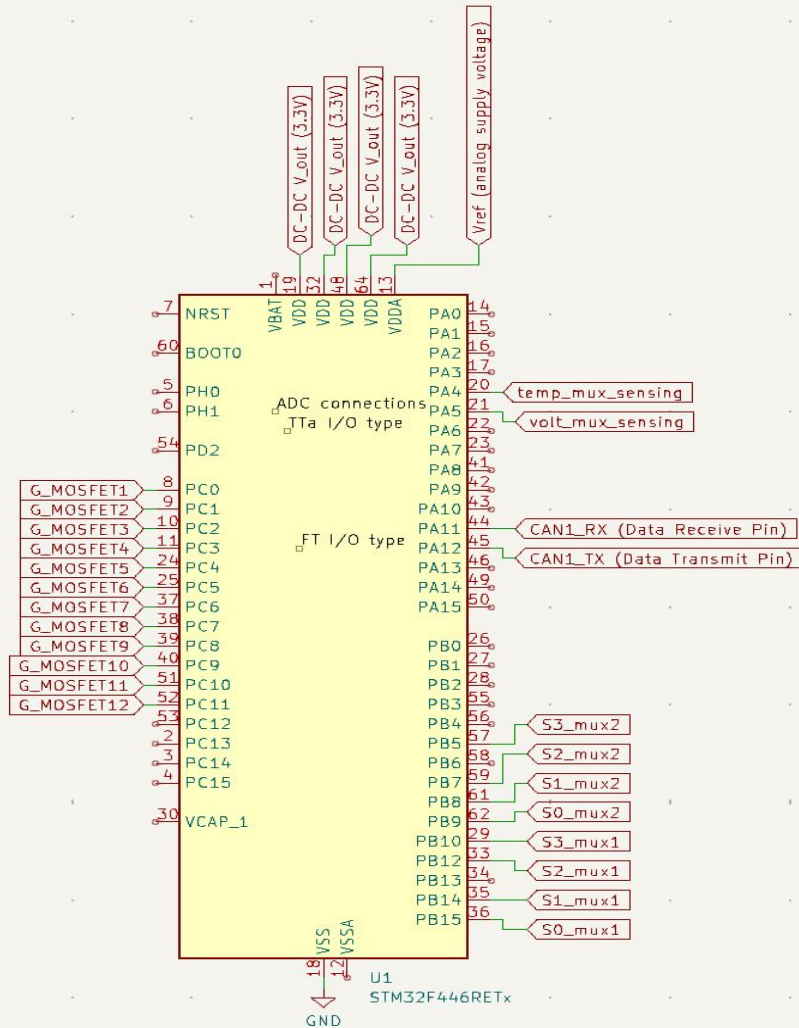- STM32F446RE
- Supplied though 3.3V from DC-DC converter
- Used TTA ADA 3.3V tolerant pins mux outputs
- Used FT 5V tolerant pins for CANbus signal inputs
- Reads temp sensing, volt sensing, and cell balancing MOSFET Gate channel reading as GPIO pins Input/Output



STM32F446RE

Pin Number : LQFP64


Pin: I/O → Input/Output pin

GPIO: General-purpose input/output


selector pins
can be used for
GPIO → I/O

Binary: 1, 0

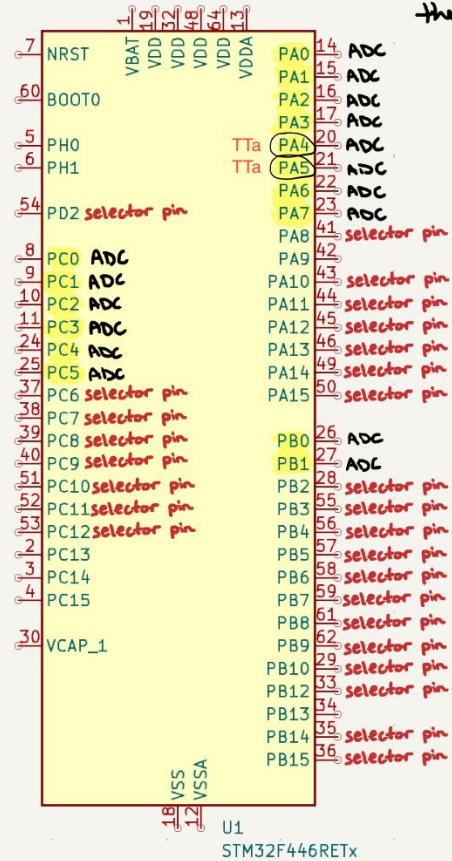
ADC pins reserved for
thermistor → mux
outputs




DC-DC Converters

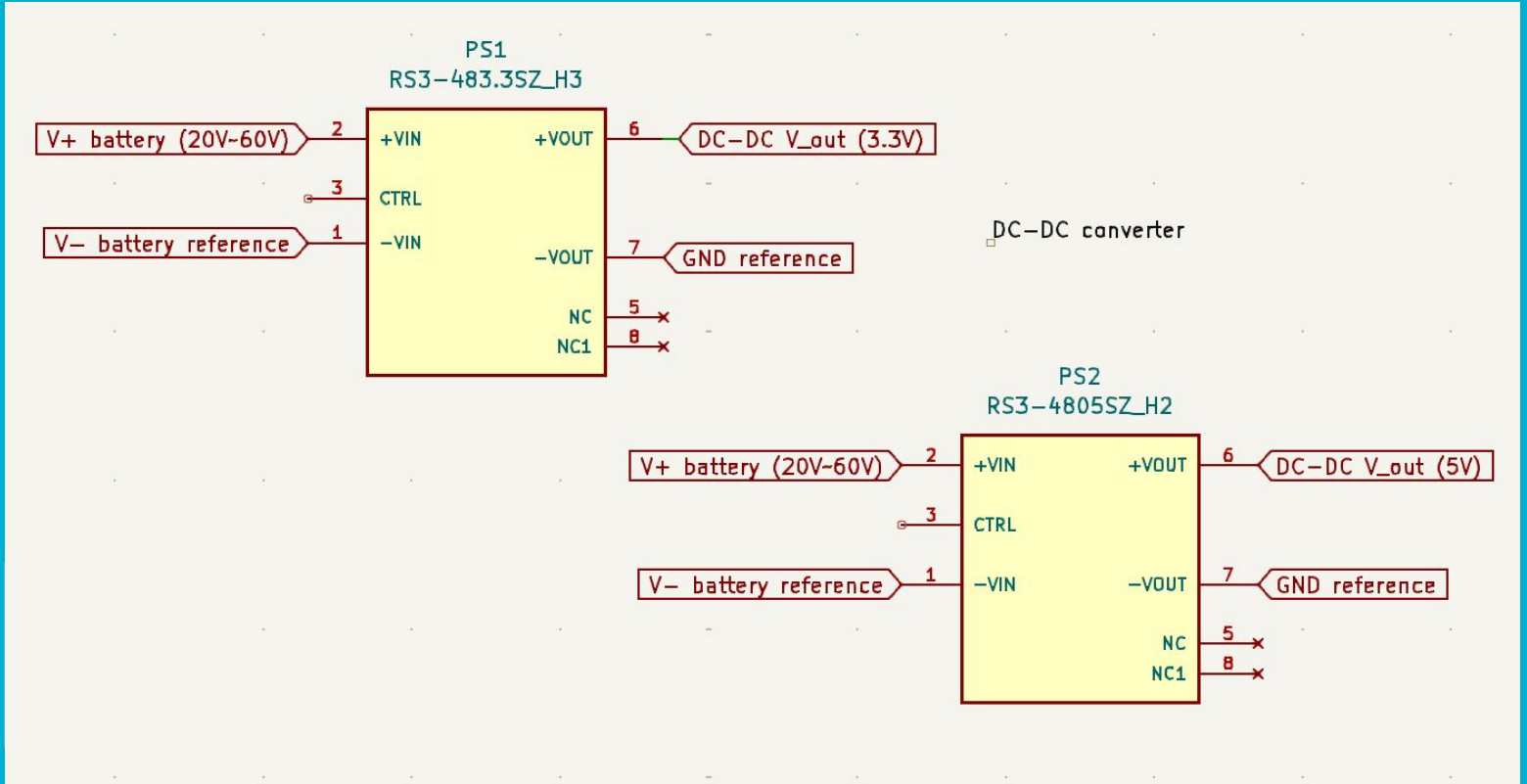

Transceiver

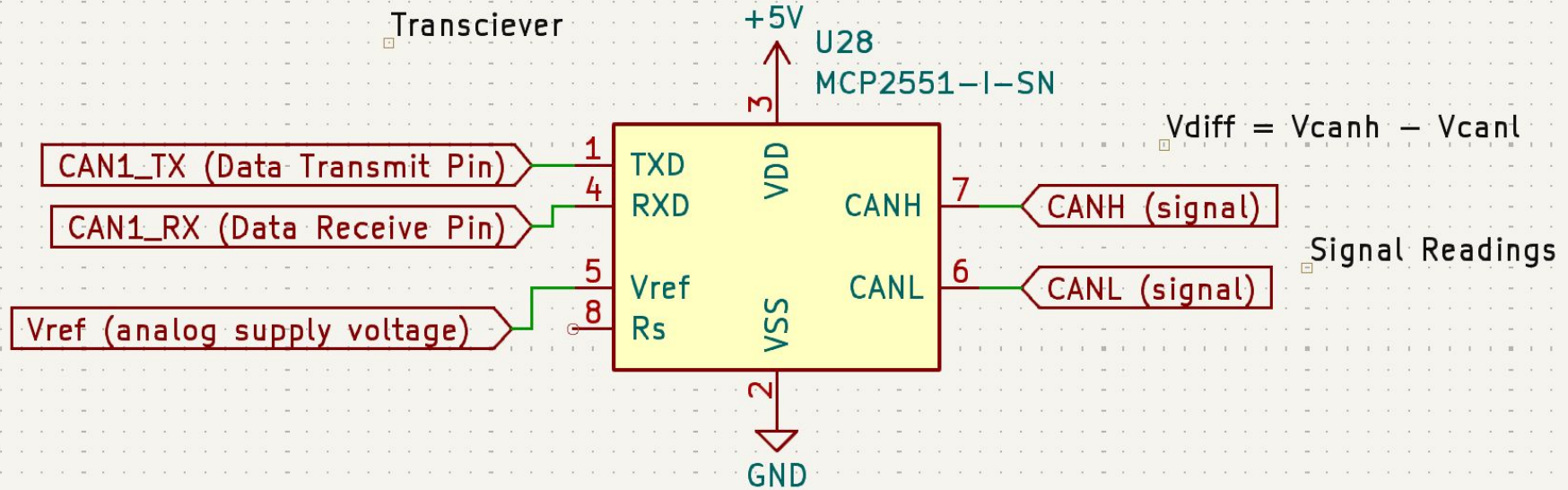

CANbus Transceiver

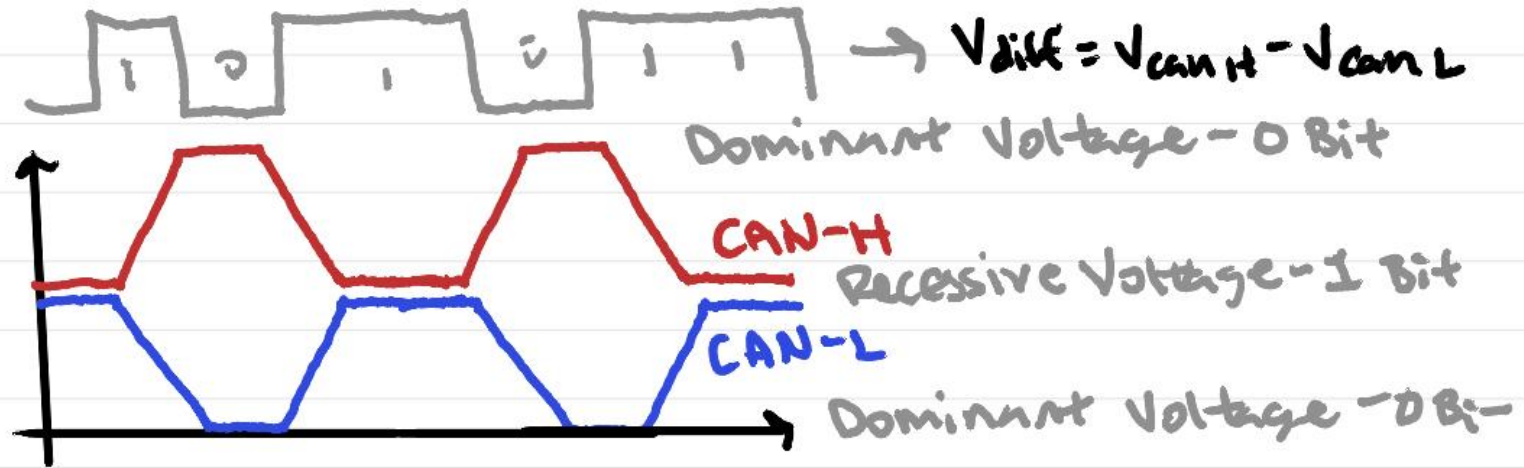

Flowchart

